

NAME Alexander J King

1. The equation for capacitive reactance is C?

- a. $\frac{1}{2\pi fL}$
- b. $2\pi fC$
- c. $\frac{1}{2\pi fC}$
- d. $2\pi fL$

2. The equation for inductive reactance is D?

- a. $\frac{1}{2\pi fL}$
- b. $2\pi fC$
- c. $\frac{1}{2\pi fC}$
- d. $2\pi fL$

3. As frequency increases capacitive reactance C?

- a. Stays the same
- b. Increases
- c. Decreases
- d. Goes negative

4. As frequency increases inductive reactance B?

- a. Stays the same
- b. Increases
- c. Decreases
- d. Goes negative

5. Reactance lies on which axis of the complex plane?

- a. X
- b. Y
- c. Z
- d. Imaginary
- e. B and D

D

6. Capacitive reactance on the complex plane is?

- a. Positive
- b. Negative

B

7. Inductive reactance on the complex plane is?
a. Positive
b. Negative

A


8. $250 - j440$ in polar notation is?
a. $-506\angle -60$
b. $506\angle -60$
c. $-506\angle 60$
d. $506\angle 60$

B

9. $25\angle 40$ in rectangular form is?
a. $-19.2 + j16.1$
b. $19.2 + j16.1$
c. $19.2 - j16.1$
d. $-19.2 - j16.1$

B

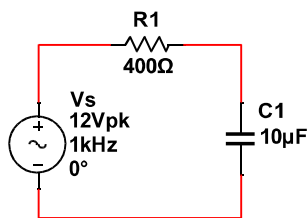10. Find Z_T , I_T and phase angle between V_s and I_T



$$Z_{eq} = z1 || z2$$

$$z1 = 400\text{ohm } z2 = 10\mu\text{F}$$

$$.5\pi * .00001 * 1000 = z2 = .0157\text{ohm}$$

$$(400 * .0157) / (400 + .0157) = Z_t = .015699\text{kohm}$$


$$z = v/i \quad i = z * v$$

$$Z = 15.699 \quad v = 12 \quad I = 15.699 * 12 = 188.388$$

$$I_t = .8660 \text{ A}$$

$$\text{Phase} = -87.7215 \text{ deg}$$

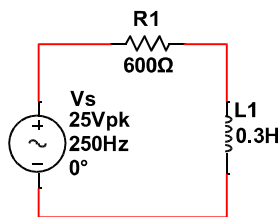11. Find Z_T , I_T and phase angle between V_s and I_T




$$Z_t = 370.6001$$

$$\text{Phase} = 51.85397$$

$$I_t = 0.27027 \text{ A}$$

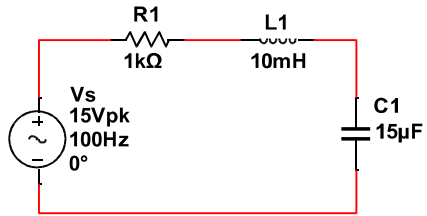12. Find Z_T , I_T and phase angle between V_s and I_T




$$Z_t = 6.6785 \text{ ohm}$$

$$I_t = 1.5902 \text{ a}$$

$$\text{Phase A} = 89.617 \text{ deg}$$

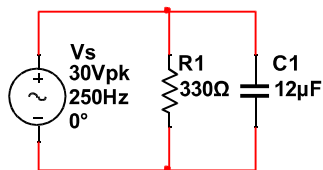13. Find Z_T , I_T and phase angle between V_s and I_T




$$Z = 52.3791 \text{ ohm}$$

$$I_t = 0.4049 \text{ Amp}$$

$$\text{Phase Angle: } -80.8671$$

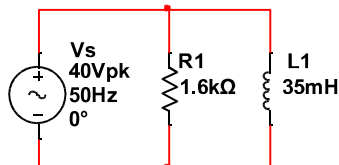14. Find Z_T , I_T and phase angle between V_s and I_T




$$Z = 10.9953 \text{ ohm}$$

$$I_t = 3.2150 \text{ amp}$$

$$\text{Phase A} = 89.6062 \text{ deg}$$

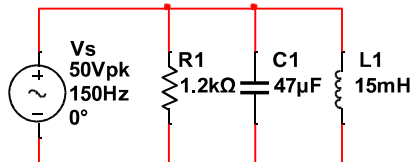15. Find Z_T , I_T and phase angle between V_s and I_T




$$Z_t = 37.8040 \text{ ohm}$$

$$\text{Phase A} = 88.1946$$

$$I_t = 0.9351 \text{ A}$$

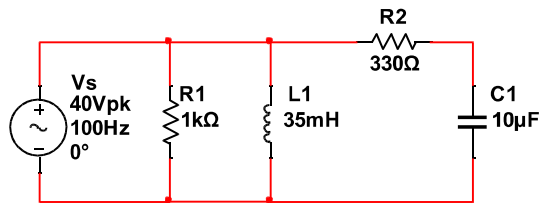16. Find Z_T , I_T and phase angle between V_s and I_T



$$Z_t = 25.3830 \text{ ohm}$$

$$I_t = 1.1141 \text{ amp}$$

$$\text{Phase A} = 84.128280377863$$